

### 3. Theory

#### 1) V-I characteristics

Applying a DC current to a component, measure the voltage across the component with a voltmeter and measure the current through the component with an ammeter. The relationship curve between the current and voltage of the component is plotted with voltage as the abscissa and current as the ordinate, and which is called the V-I (volt-ampere) characteristic curve of the component. Components with a linear V-I characteristic curve are called linear components, such as resistors. Components with a non-linear V-I characteristic curve are called non-linear components, such as diodes and transistors.

In addition to the voltage and current, the V-I characteristics of some components also change regularly with the change of a certain physical quantity, such as temperature, light intensity, magnetic field strength, etc. This is the sensing element for various physical quantities. .

According to Ohm's law, the relationship among resistance  $R$ , voltage  $U$ , and current  $I$  is follows:

$$R = U/I . \quad (1)$$

The resistance value of the element  $R_x$  can be calculated by measuring values  $U$  and  $I$  using voltmeter and the ammeter. However, the  $R$  value of a non-linear element is a variable, so its resistance value is related to its specific operating voltage (or current).

There are two ways to express the resistance of nonlinear components. One is called static resistance (or DC resistance), expressed by  $R_D$ ; the other is called dynamic resistance, expressed by  $r_D$ , which is equal to the ratio between the amounts of voltage change and current change near the operating point. The dynamic resistance can be obtained by the V-I curve, as shown in Figure 1, where the static resistance  $R_D = U_Q/I_Q$  and the dynamic resistance  $r_D = \Delta U_Q/\Delta I_Q$  at point  $Q$  .

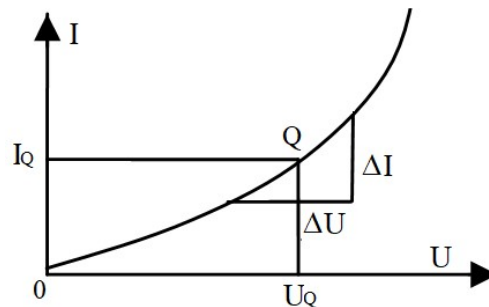


Figure 1 Dynamic resistance representation

When measuring the V-I characteristics, a certain system error will be introduced due to the internal resistance of the voltmeter and ammeter. Because of high internal resistance of the digital voltmeter and small internal resistance of the digital ammeter, the system error is small and it is ignored in this experiment.

#### 2) Characteristics of semiconductor diode

The semiconductor diode is a commonly used non-linear element. Figure 2(a) is the circuit symbol. The main characteristic of the diode is unidirectional conductivity. Its V-I

characteristic curve is shown in Figure 2 (b). When the forward current or forward voltage is small, the current is small. When the forward voltage increases to a certain value, the forward current increases significantly and thereafter approximately increases in linear. Extend this straight line in the opposite direction to the horizontal axis, the intersection point  $U_D$  is called the forward threshold voltage. After forward conduction, the forward voltage drop is about 0.2-0.3 V for a germanium tube, and about 0.6-0.8 V for a silicon tube. When the reverse voltage exceeds a certain value  $-U_b$ , the current increases sharply. This situation is called breakdown, and  $U_b$  is the breakdown voltage.

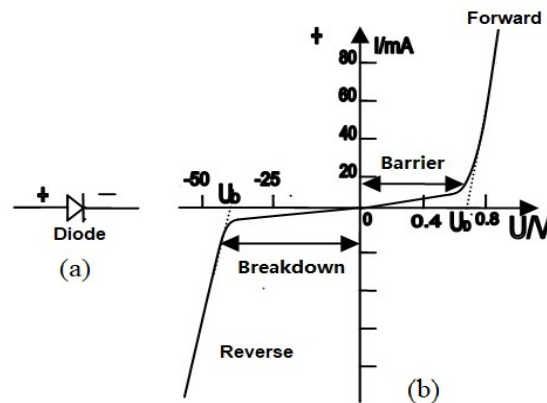


Figure 2 (a) Symbol of diode, (b) V-I characteristic curve

### 3) Characteristics of Zener diode

The zener diode is a special silicon diode. Its symbol is shown in Figure 3 (a); its V-I characteristic curve is shown in Figure 3 (b). It has a wide current range in the reverse breakdown region and the V-I curve is cliffy straight line. This straight line intersects the horizontal axis at  $U_w$ .

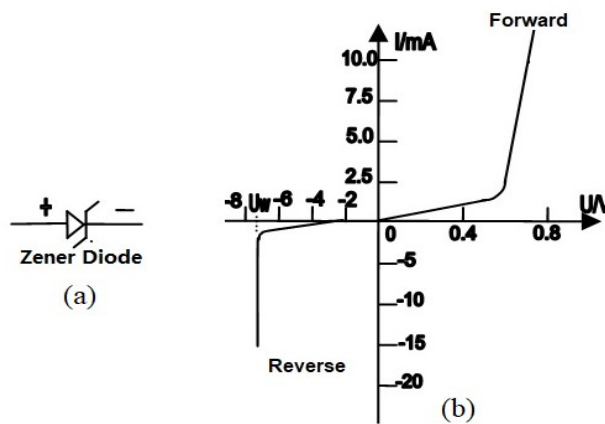


Figure 3 (a) Symbol of Zener diode, (b) V-I characteristic curve

For ordinary diodes, the current increases sharply after the breakdown voltage and when the current exceeds the limit value  $-I_s$ , the diode will be burned. For Zener diode, the reverse breakdown is reversible, i.e. after removing the reverse voltage, the Zener diode returns to normal state (but if the reverse current exceeds the allowable range, the Zener diode will also be burned due to thermal breakdown). Therefore, the working current of the Zener diode should be set according to the allowable working current for normal operation.

The main parameters of the Zener diode include regulation voltage  $U_w$ , dynamic resistance  $r_D$  (the smaller  $r_D$ , the better the voltage regulation performance), the minimum regulated current  $I_{min}$ , the maximum regulated current  $I_{max}$ , and the maximum dissipated power  $P_{max}$ .

#### 4) Characteristics of light emitting diode

The core of light emitting diodes (LED) is a PN junction. Therefore, it has the general PN junction V-I characteristics, namely forward conduction, reverse cut-off, and breakdown characteristics. The symbol of LED is shown in Figure 4 (a), which is mainly because it has light-emitting characteristic. Under the forward voltage, electrons are injected into the P region from the N region, and holes are injected into the N region from the P region. The minority carrier enters the opposite region, at this time, the electrons entering the P region recombine with the holes in the P region, and the holes entering the N region recombine with the electrons in the N region, and radiate excess energy in the form of light, which is the basic working principle of LED, as shown in Figure 4 (b).

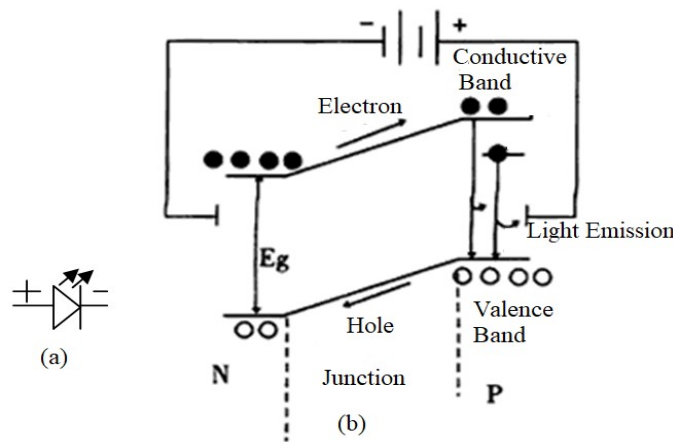


Figure 4 (a) LED symbol, (b) LED basic working principle

Theory and practice have proved that the peak wavelength  $\lambda$  of light emission is related to the width  $E_g$  of the semiconductor forbidden band in the light-emitting region,  $\lambda \approx 1240 / E_g(nm)$ , the unit of  $E_g$  is electron volt (eV).

The main parameters of the LED are follows:

- Maximum forward current  $I_{Fm}$ : The maximum forward DC current allowed. The LED will be damaged if it exceeds this value.
- Forward working current  $I_F$ : refers to the forward current value when the LED normally emits light. In actual use, the  $I_F$  should be selected below  $0.6 \cdot I_{Fm}$  according to the brightness needs.
- Forward working voltage  $V_F$ : The forward working voltage is measured at a given forward current. Generally at  $I_F = 20 \text{ mA}$ ,  $V_F$  is  $1.4 \sim 3 \text{ V}$ .
- Maximum reverse voltage  $V_{Rm}$ : The maximum reverse voltage allowed to be applied, and the LED may be damaged by breakdown if it exceeds this value.
- Allowable power consumption  $P_m$ : The maximum value of the product of the forward DC voltage applied to both ends of the LED and the current flowing through it. Beyond this value, the LED may be damaged by heat.

- f) V-I characteristic: The relationship between LED voltage and current, as shown in Figure 5.

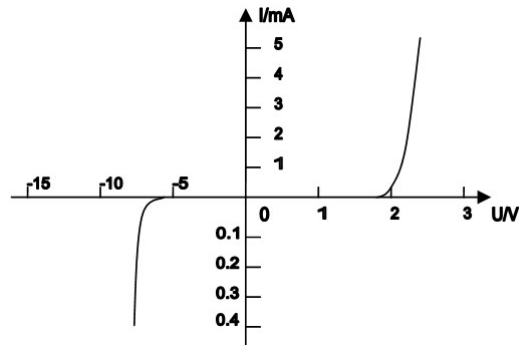


Figure 5 Relationship between voltage and current of LED

- g) Spectral distribution and peak wavelength: The light emitted by a certain LED is not a single wavelength, and its wavelength is generally shown in Figure 6 (for example).

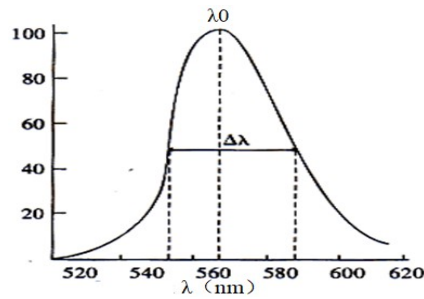


Figure 6 Example of spectral distribution and peak wavelength of LED

- h) Spectral half-width  $\Delta\lambda$ : It represents the spectral purity of the LED, which refers to the interval between two wavelengths corresponding to 1/2 peak light intensity.

\* Parameters such as luminous intensity, divergence angle and viewing angle are also important, but not studied in this experiment.